


ANALOG HEART

HEART ECG MONITOR




INTRODUCTION

- An ECG (Electrocardiogram) monitor measures the electrical activity of the heart to detect abnormalities in heart rhythm.
- It records the heart's electrical signals using electrodes placed on the body.
- The goal of our project is to design and build a high precision ECG monitor using analog components.
- The device will amplify and filter the heart's electrical signals to produce a readable ECG waveform.

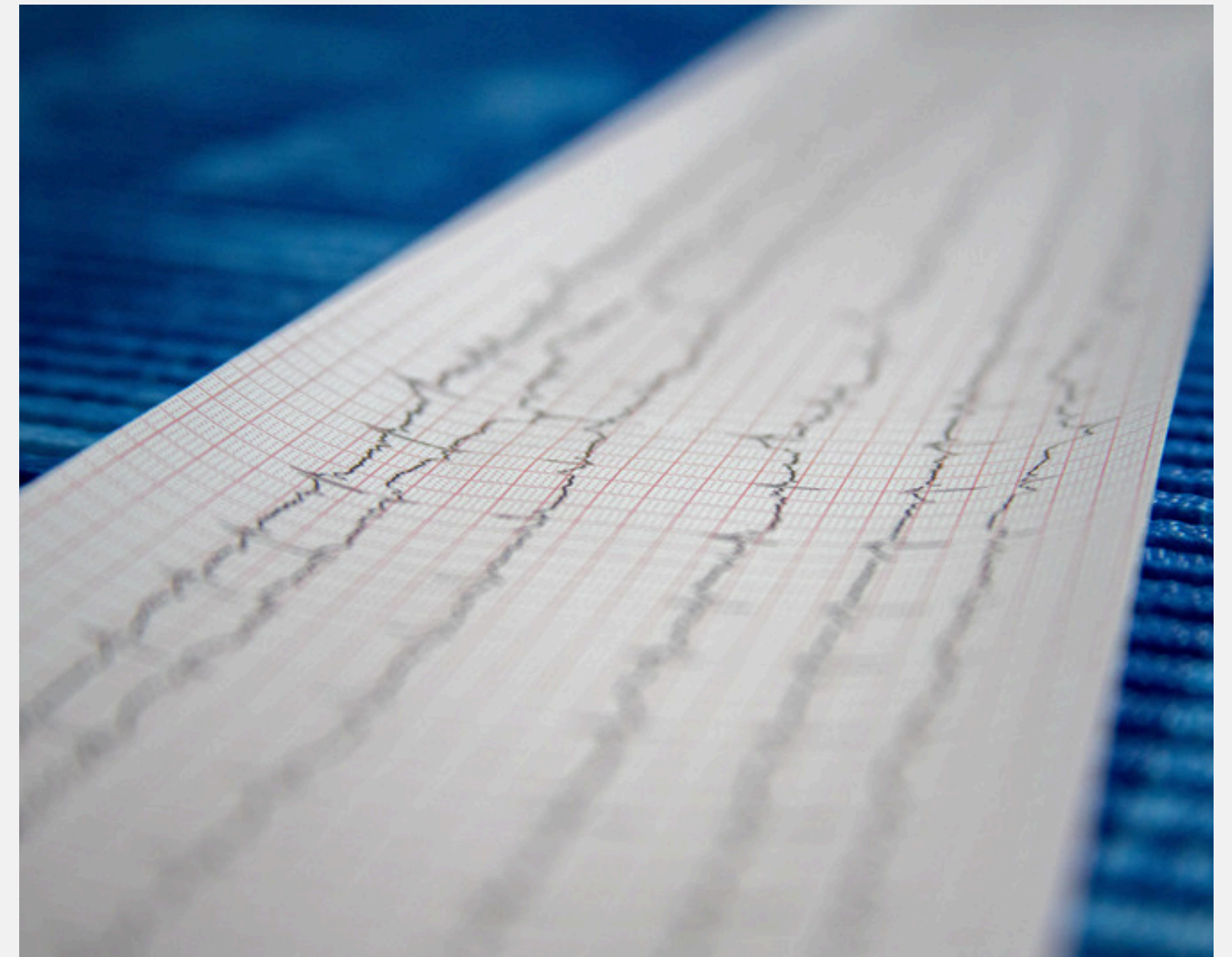


SYSTEM ARCHITECTURE

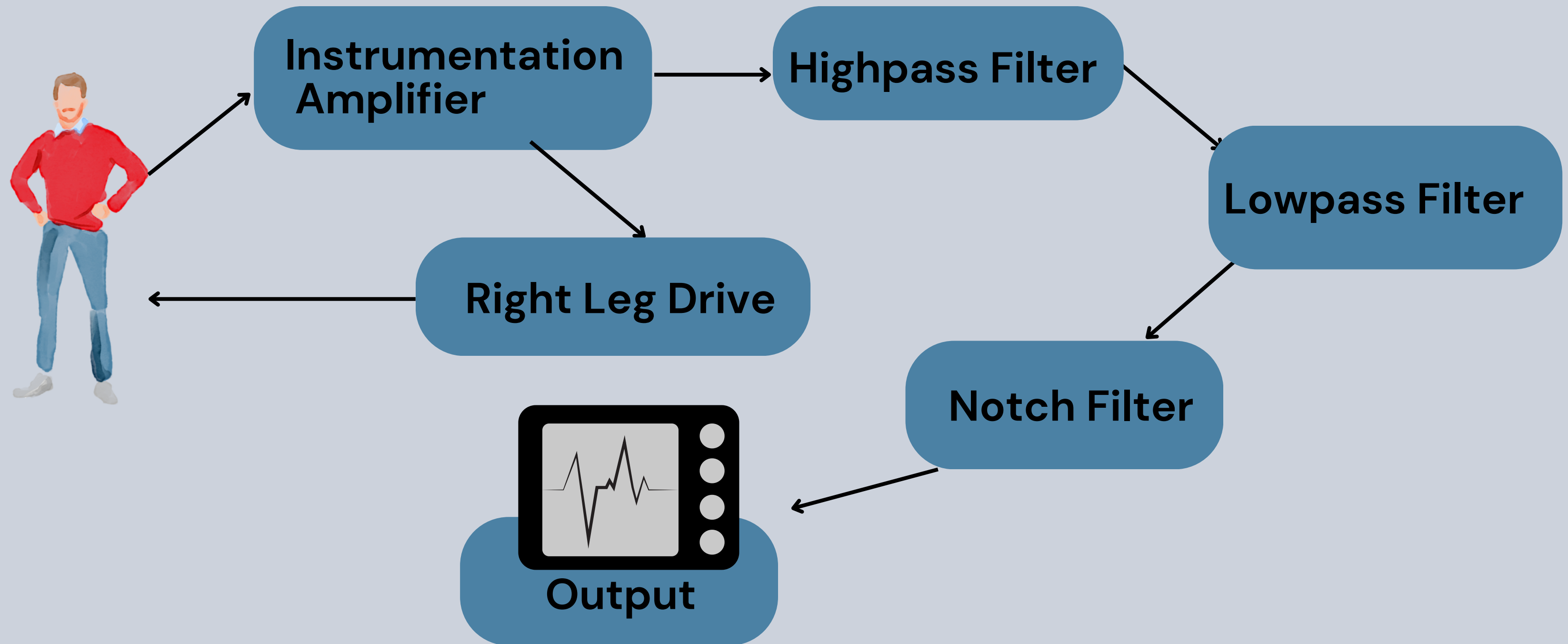

INSTRUMENTATION AMPLIFIER

- Used to amplify the small differential voltage produced by the heart's electrical activity while rejecting common noise

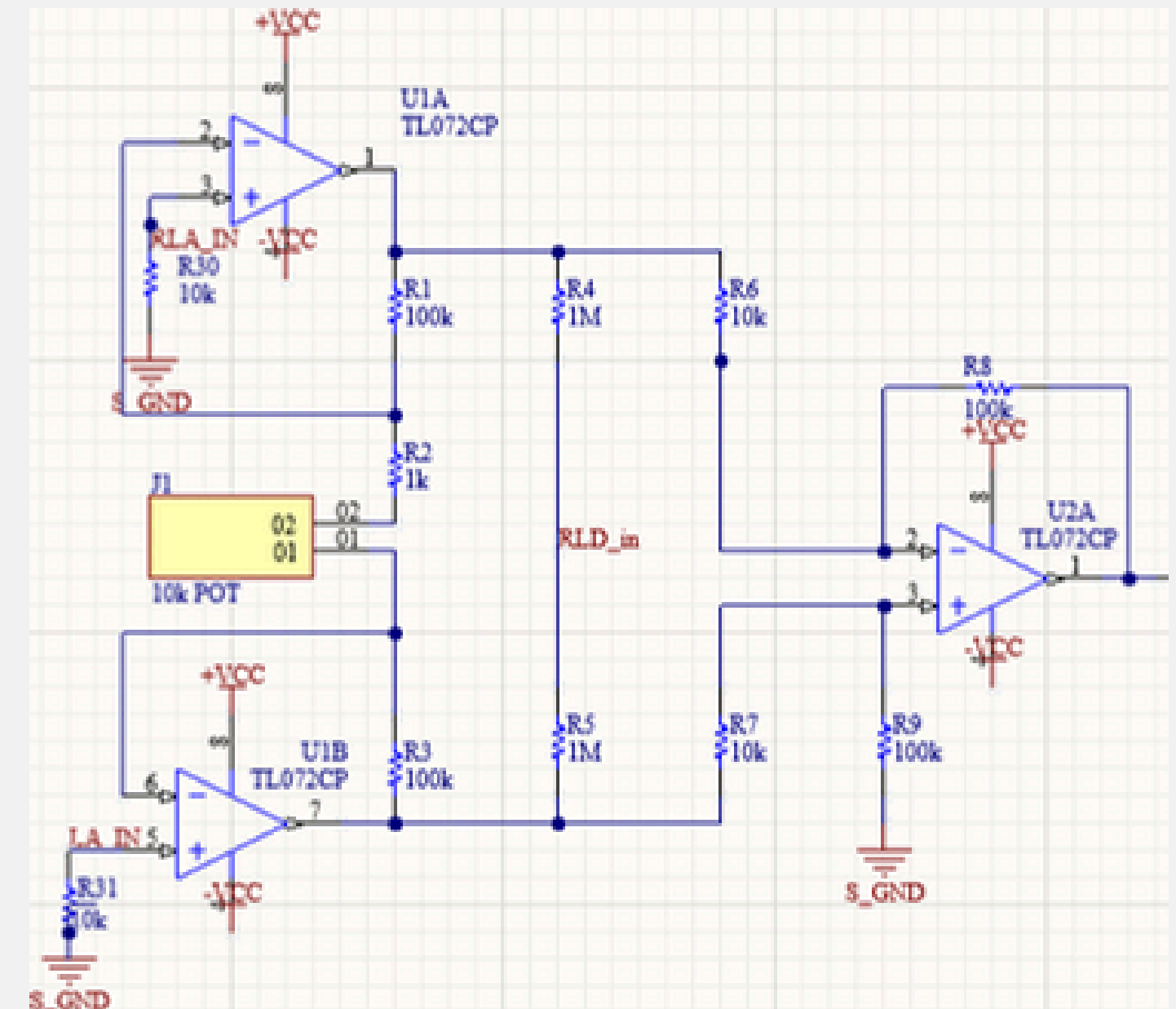- Gain –
$$1 + \frac{2R_1}{R_{\text{var}}} = 1 + \frac{2 \times 100}{R_{\text{var}}}$$




HIGHPASS FILTER

- Used to remove low-frequency noise and the DC offset from the ECG signal, such as baseline wander caused by patient movement or breathing.
- Gain – 17.25
- Cutoff frequency – 0.15 Hz

$$G = 1 + \frac{R_{13}}{R_{12}}$$


$$f_c = \frac{1}{2\pi RC}$$

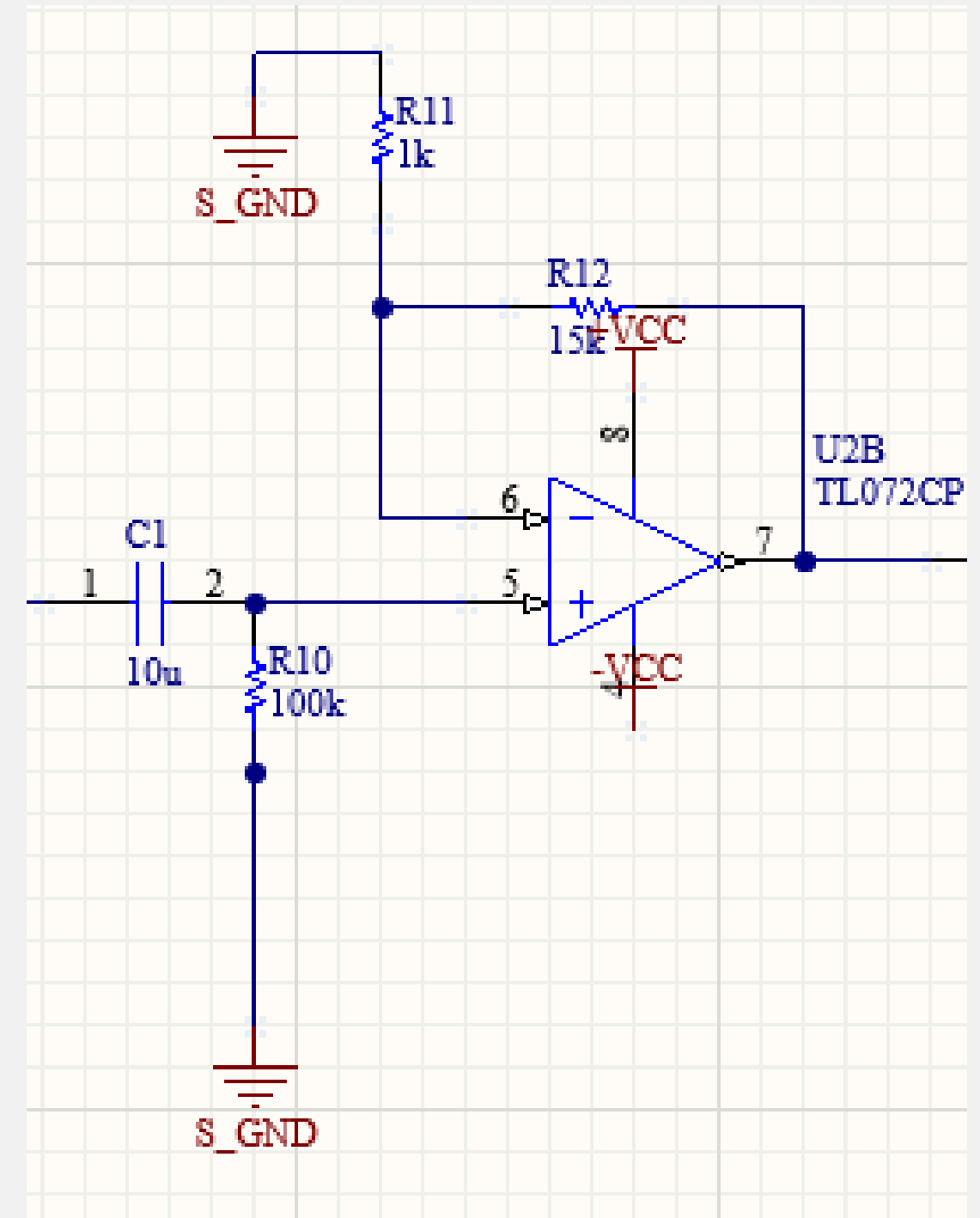


LOWPASS FILTERS

- Used to eliminate high-frequency noise from the ECG signal, such as muscle artifacts or electromagnetic interference.
- Fifth order bessel filter is used.
- Cutoff frequency – 164.15 Hz
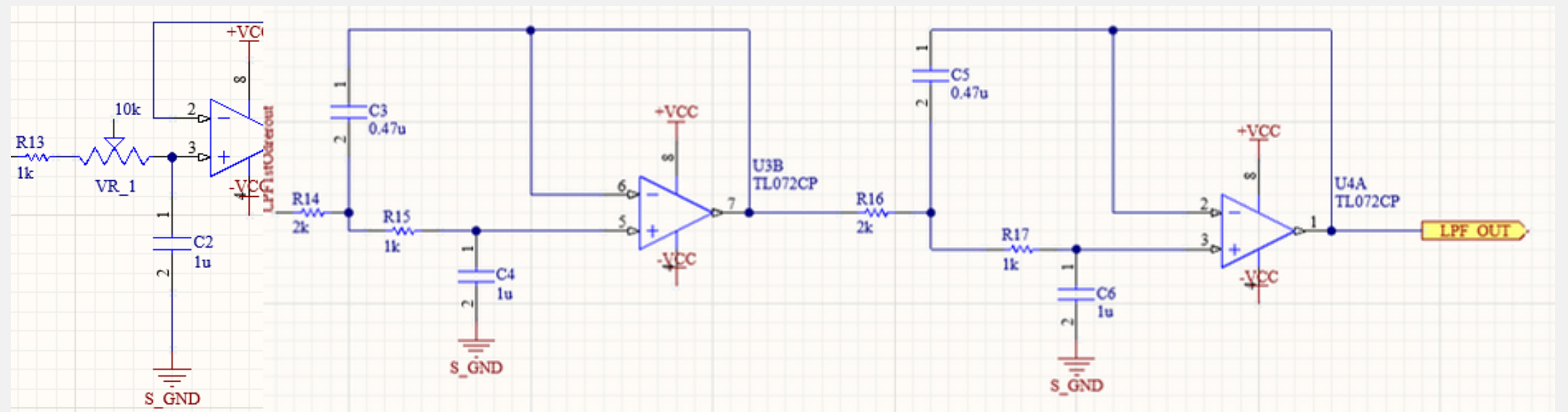
$$f_c = \frac{1}{2\pi \sqrt{R_{21} R_{24} C_6 C_7}}$$
$$= \frac{1}{2\pi \sqrt{2 \times 1 \times 0.47 \times 1}}$$




LOWPASS FILTERS

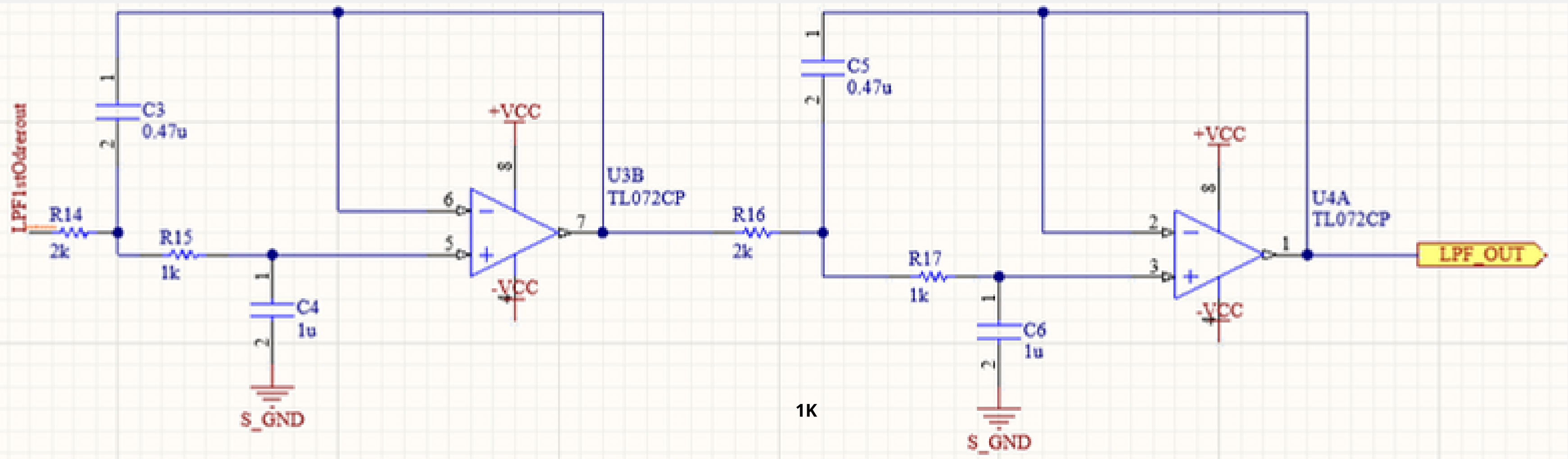

NOTCH FILTER


- Used to eliminate power line interference, which typically occurs at 50 Hz
- Twin-T Notch Filter with feedback is used.
- Notch frequency – 50Hz
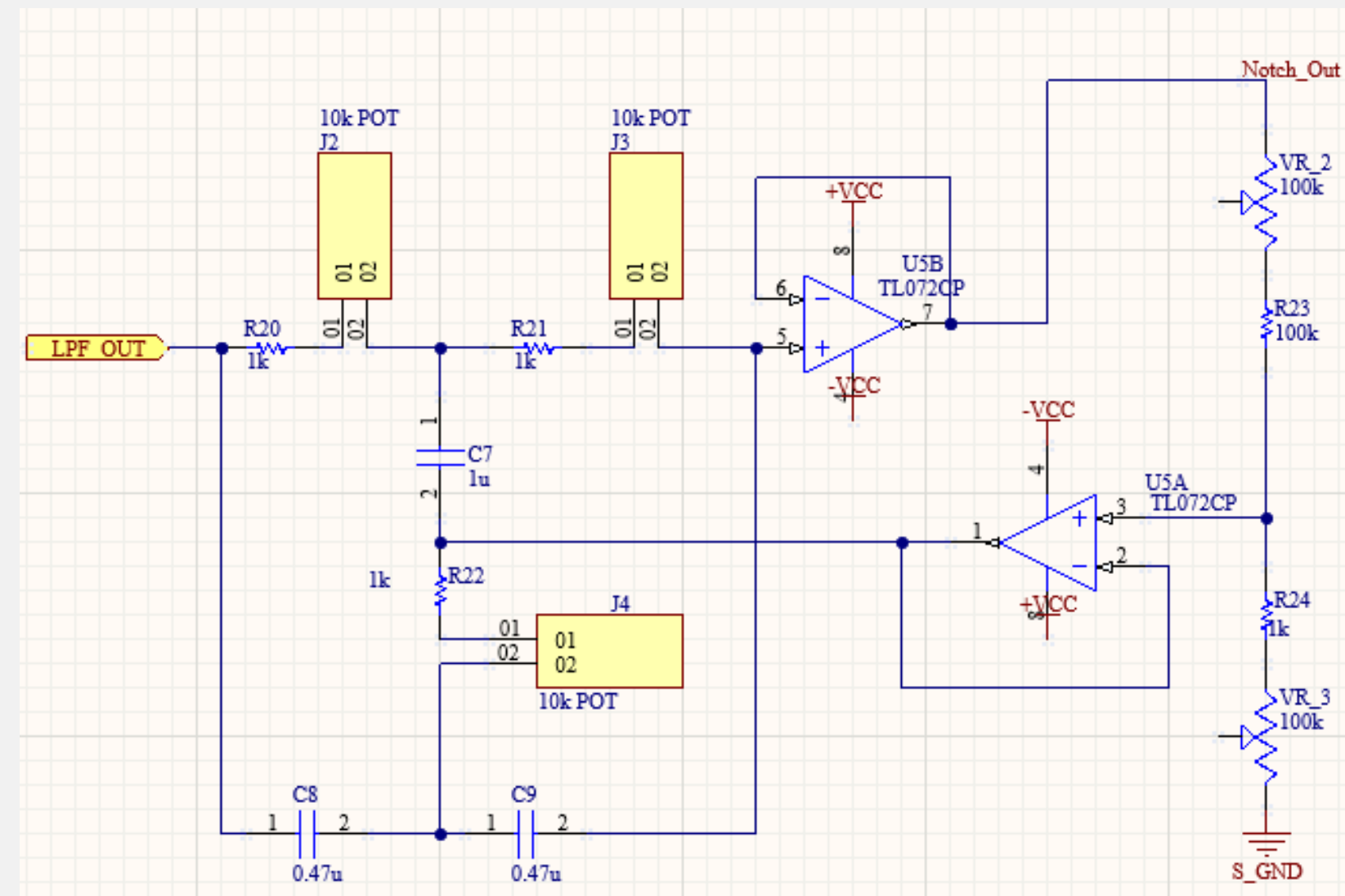
$$f_n = \frac{1}{2\pi RC \cdot 10^3}$$
$$= \frac{1}{2\pi \times 6.8 \times 0.47}$$



RIGHT LEG DRIVE

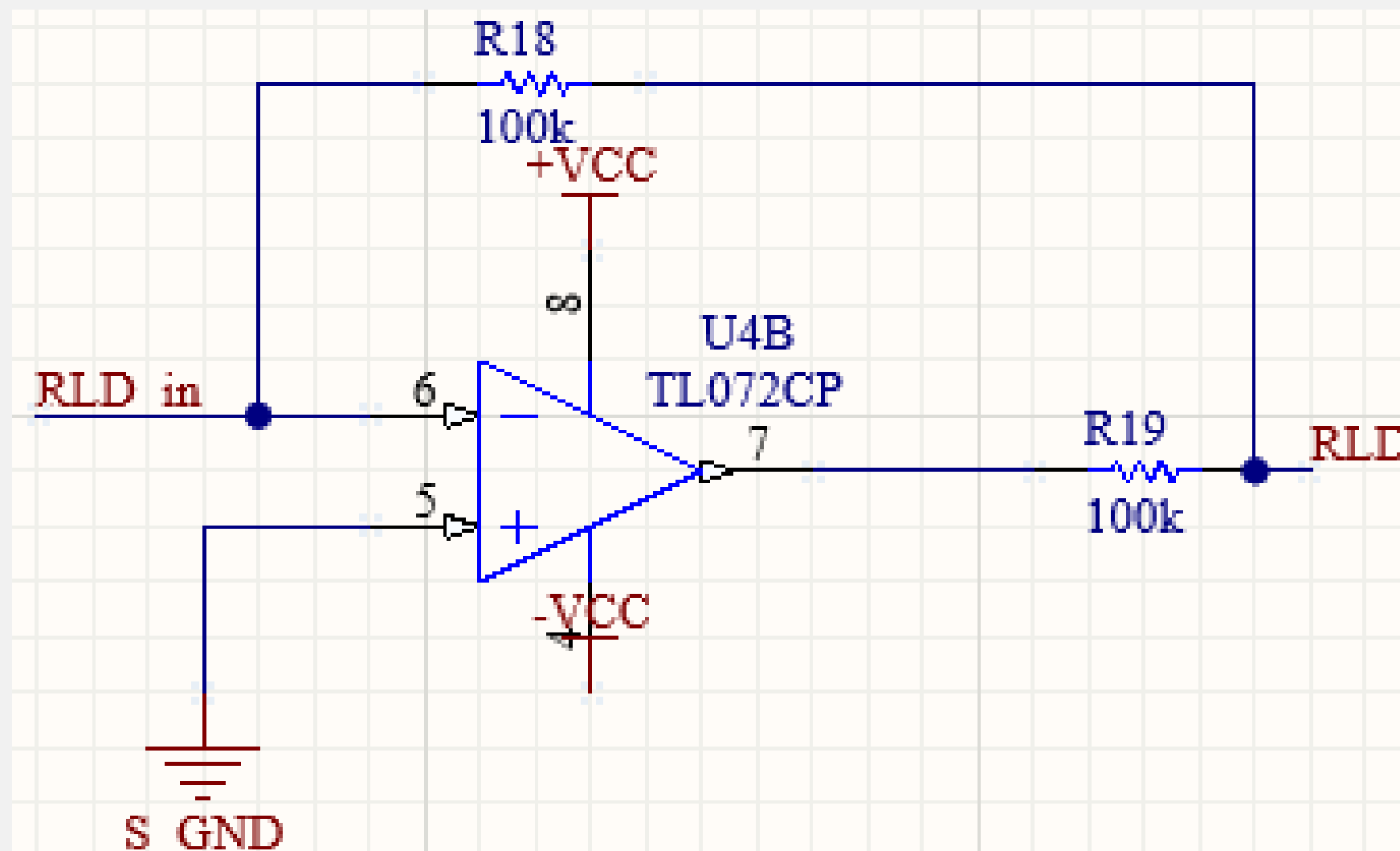
- Used to reduce common-mode interference (such as 50/60 Hz noise) by stabilizing the patient's body potential.



POWER CIRCUIT


- We are using a boost converter TPS61040 to produce +12V and -12V to power up the Opamps.
- Also we have used a DC-DC booster to power up the ESP-32 module after regulating through ams1117-3.3 regulator.
- Furthermore we have proposed to use to a Lipo Battery to make the device portable and a charging module to make it user friendly for the user to recharge.

SIMULATION

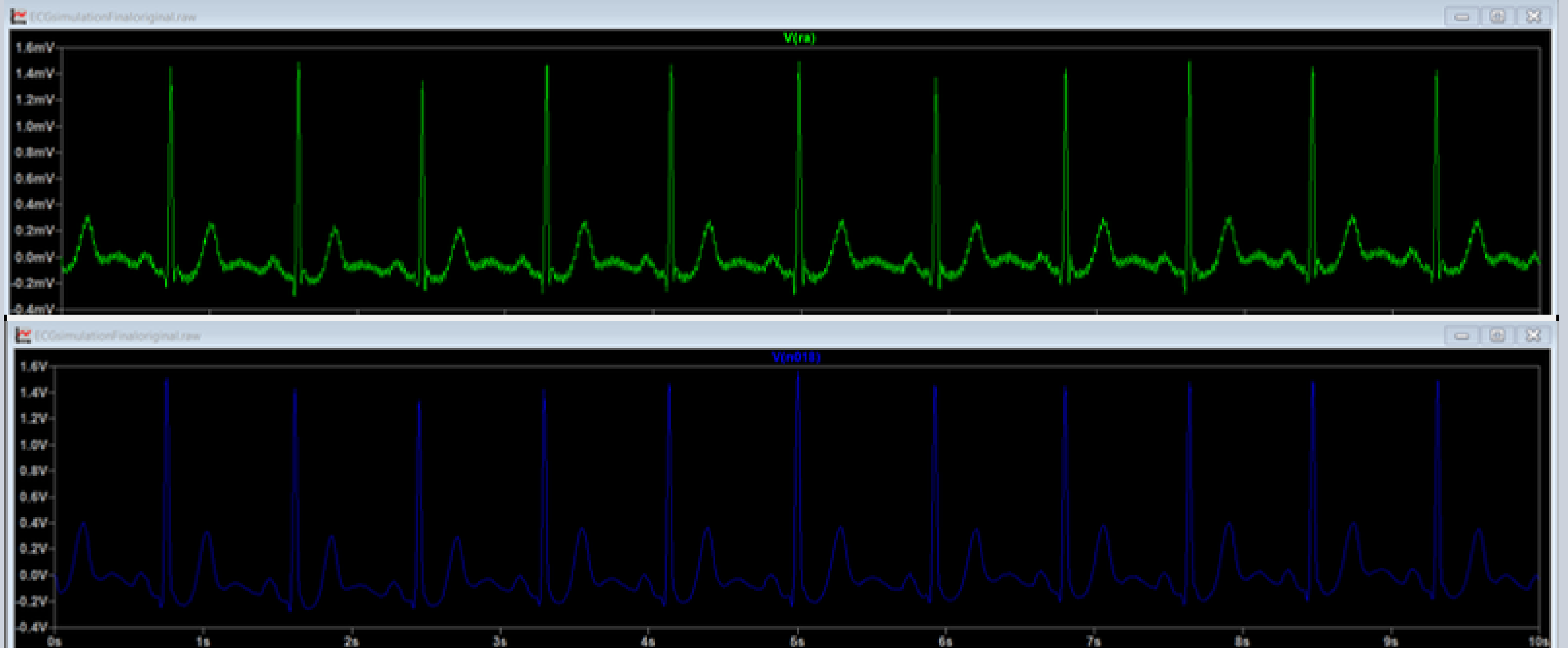

COMPONENT SELECTION - JUSTIFICATION

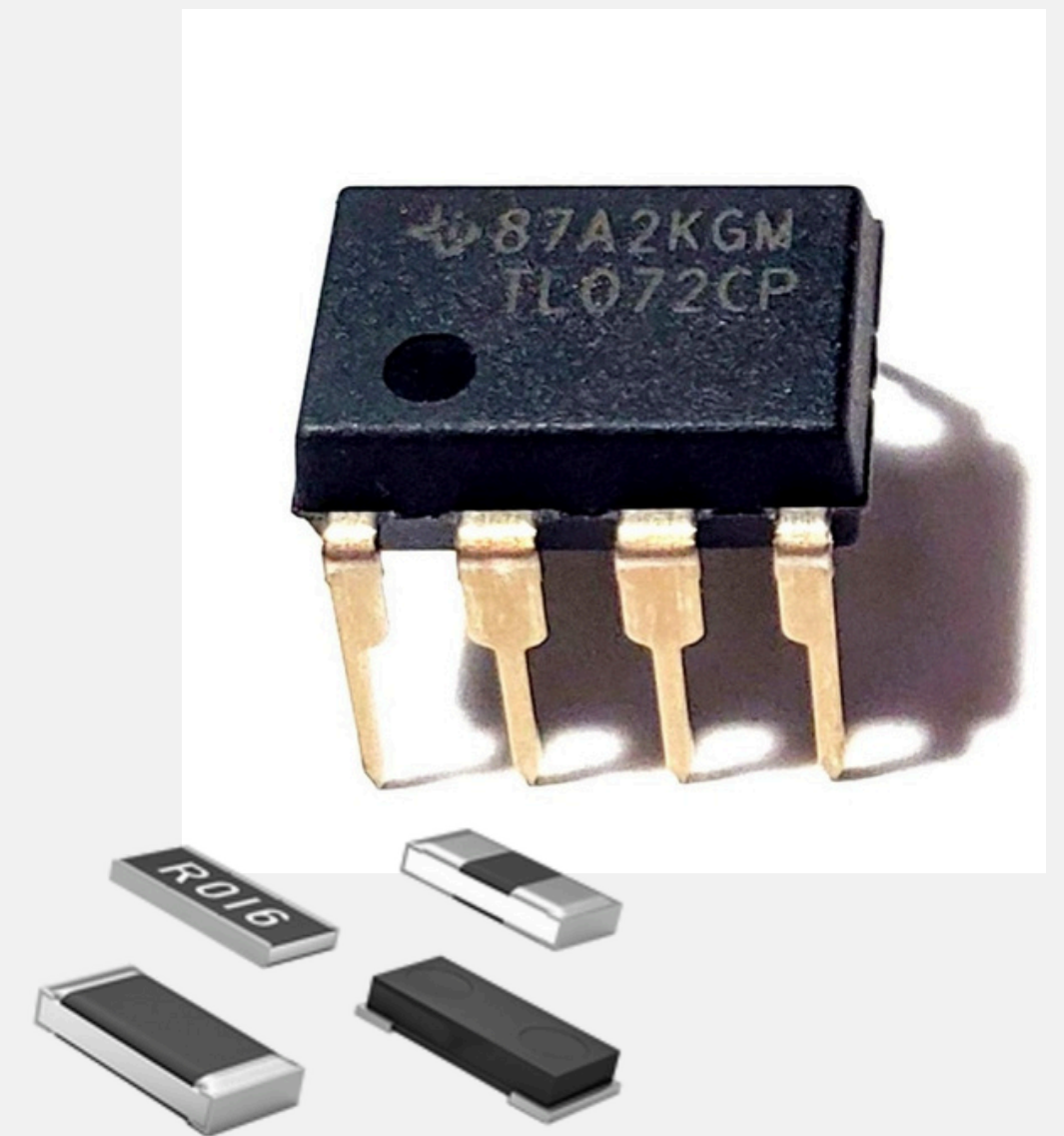- TL072 Op-Amp:
 - Low noise, high input impedance, and low power, good for ECG signals.
 - Dual op-amps reduce PCB space and cost.
- SMD Resistors and Capacitors:
 - Compact size for portable design.
 - Better signal integrity and noise performance.
- External Potentiometers:
 - Enables real-time filter adjustment for signal clarity.
 - Adjustable cutoff frequencies




COMPONENT SELECTION – JUSTIFICATION


- LiPo Battery
 - Portability: Enables wearable, mobile ECG monitoring.
 - Battery-Powered Operation: Eliminates direct connection to mains power, significantly reducing 50 Hz interference from power line noise.
 - High Energy Density: Provides long-lasting power in a small form factor.
 - Rechargeable: Reduces costs and environmental impact.
 - Stable Output: Ensures consistent performance for sensitive circuits.
 - Safety: Built-in protection against overcharging and overheating.




CIRCUIT TESTING

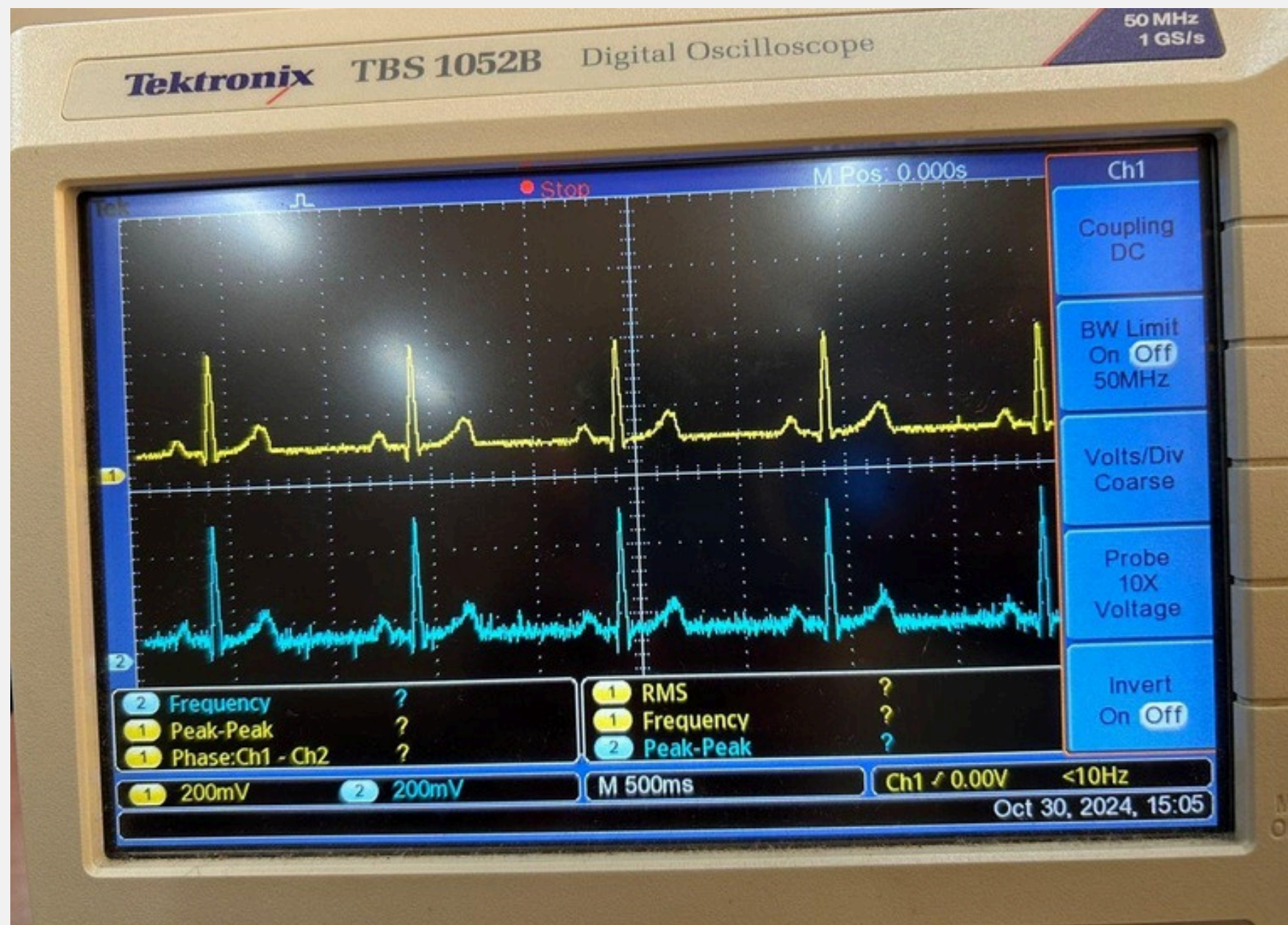


Breadboard circuit - fluke

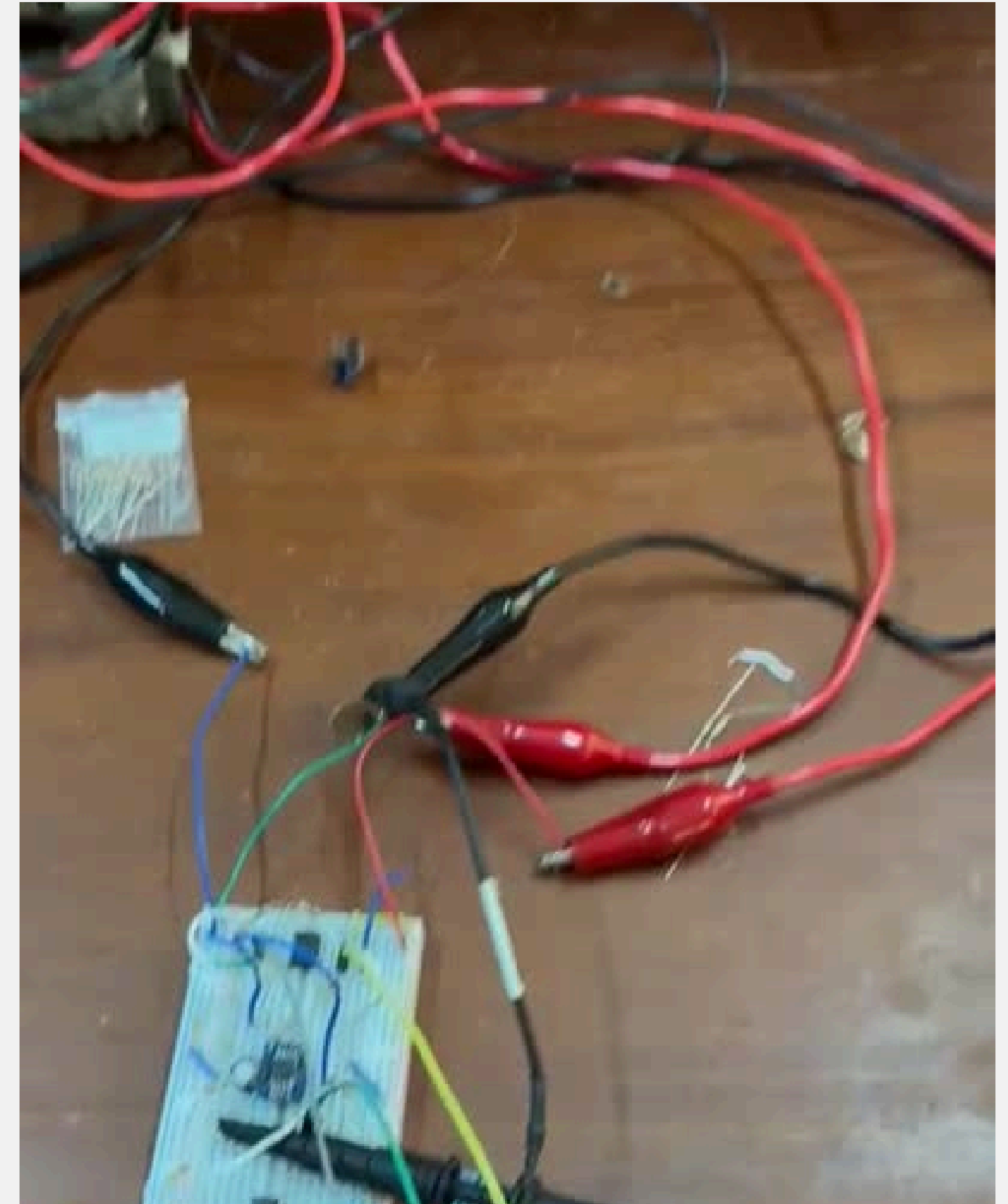


CIRCUIT TESTING

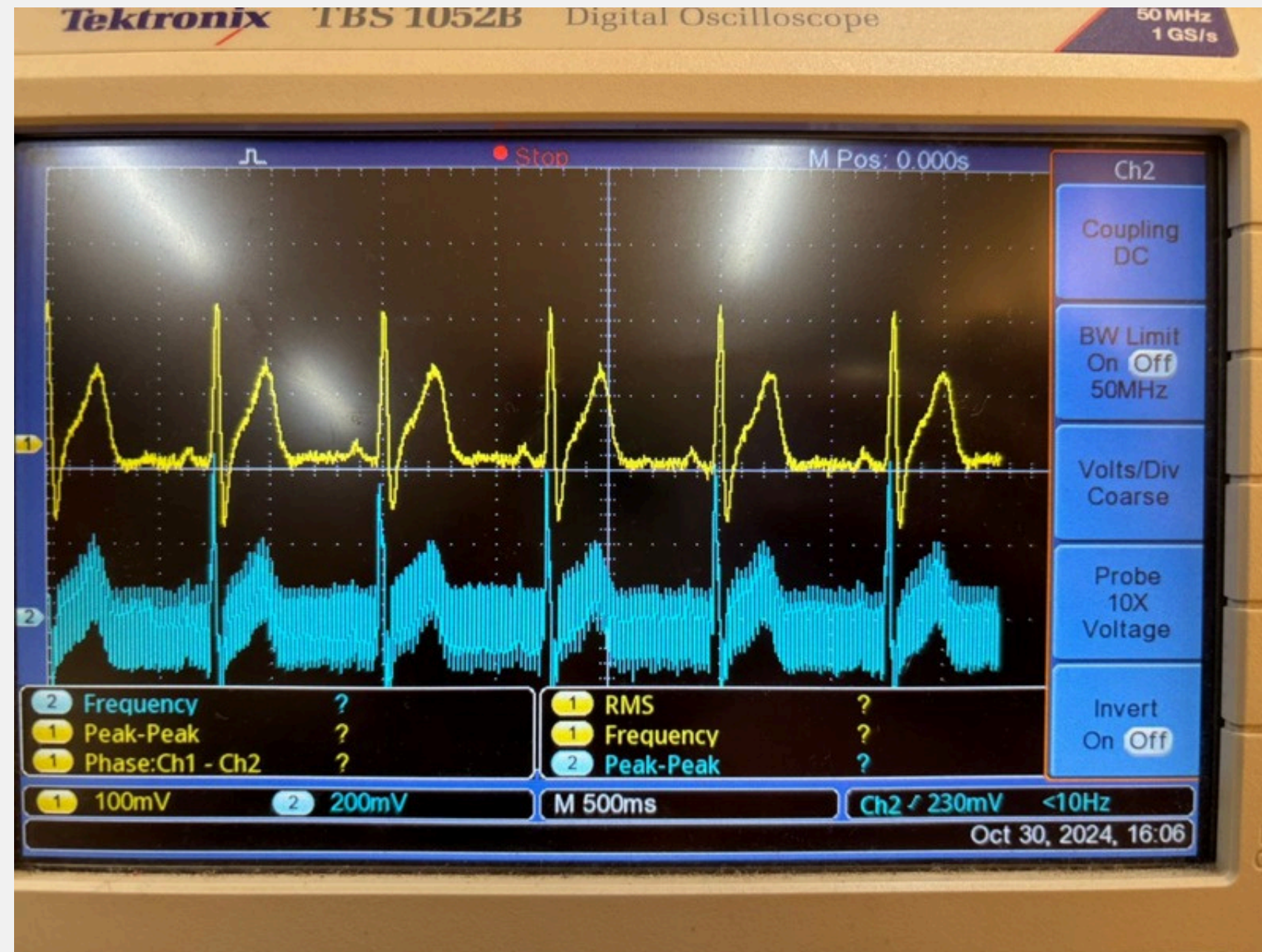


Breadboard circuit - human testing

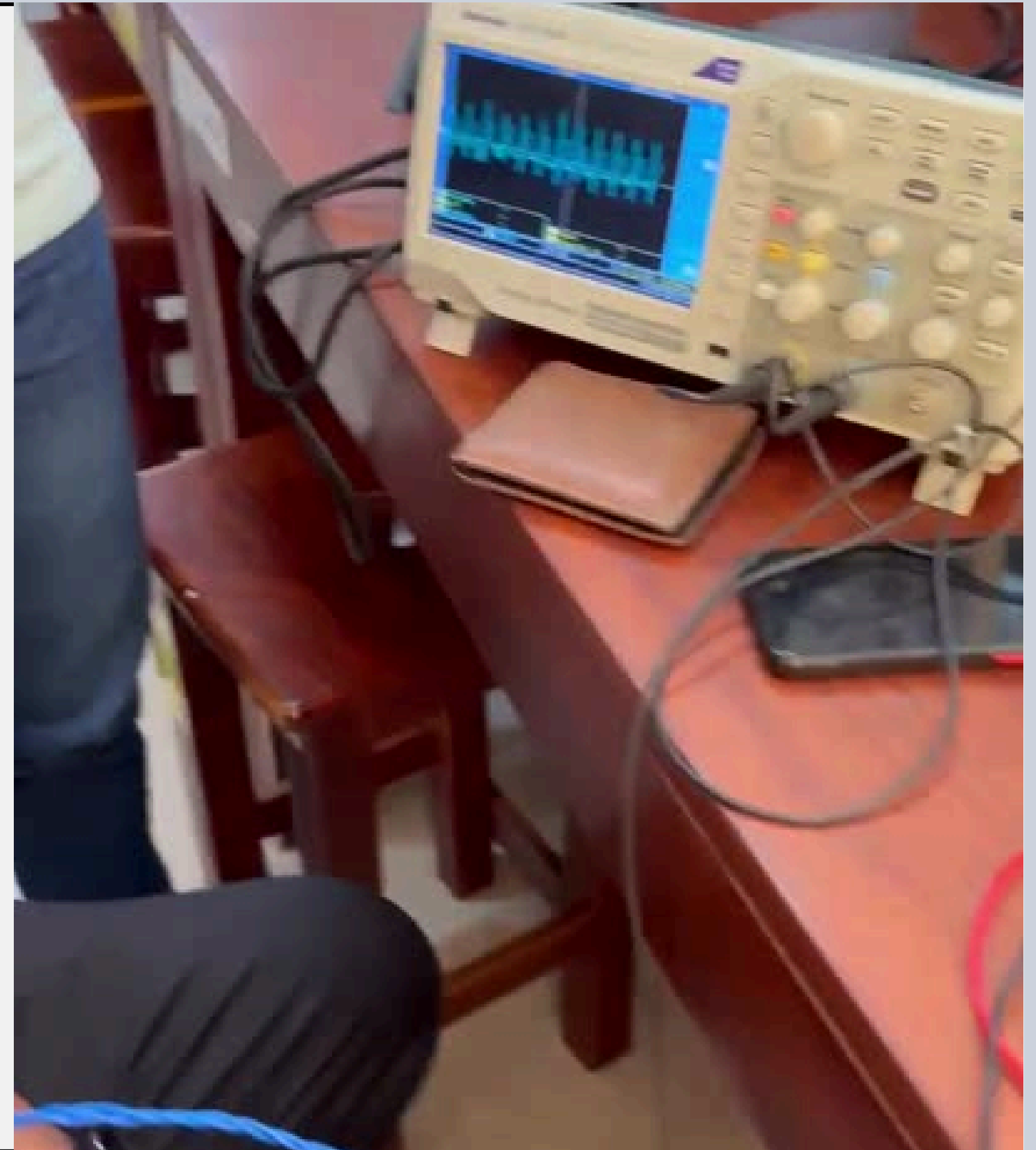


CIRCUIT TESTING

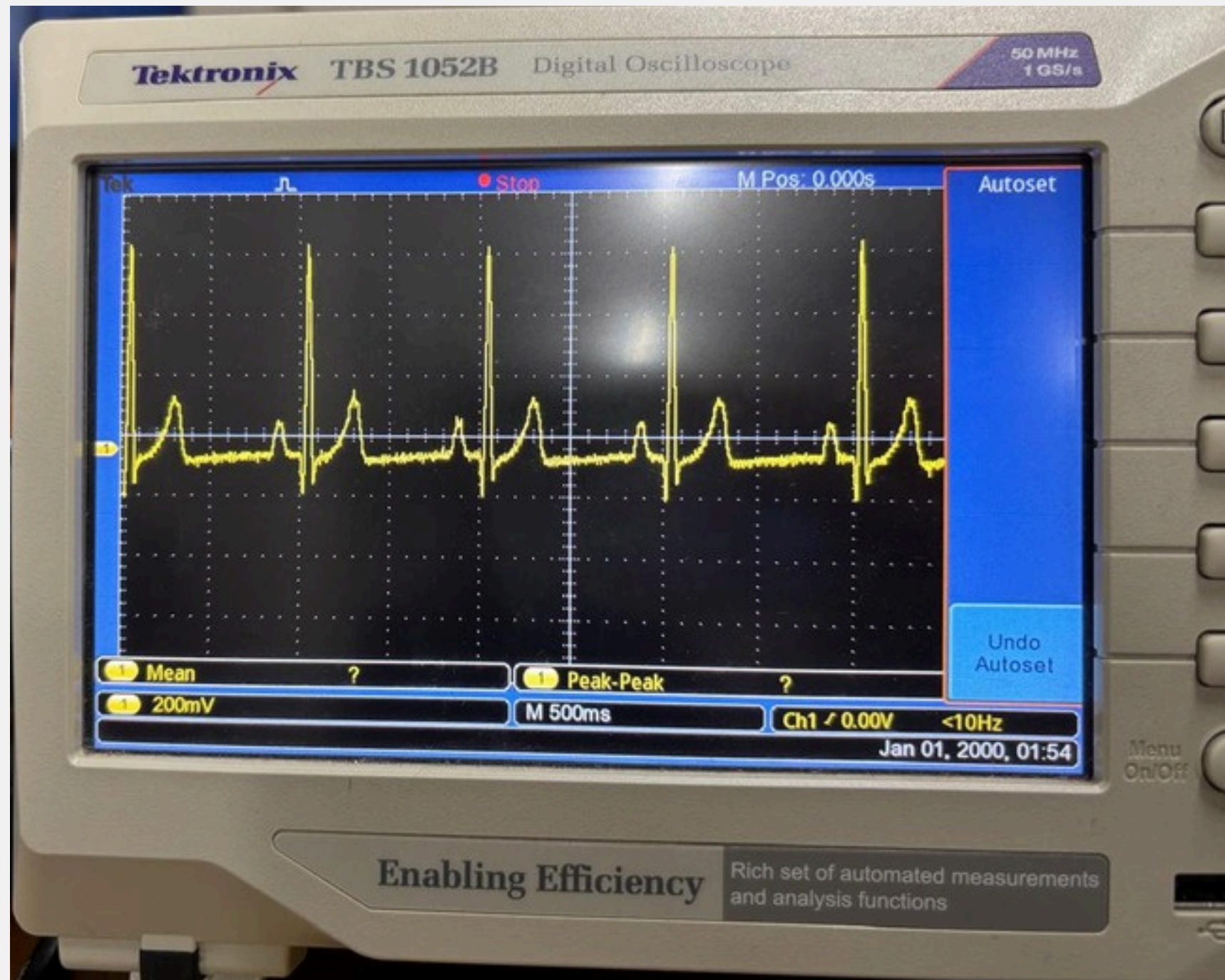


PCB circuit - fluke

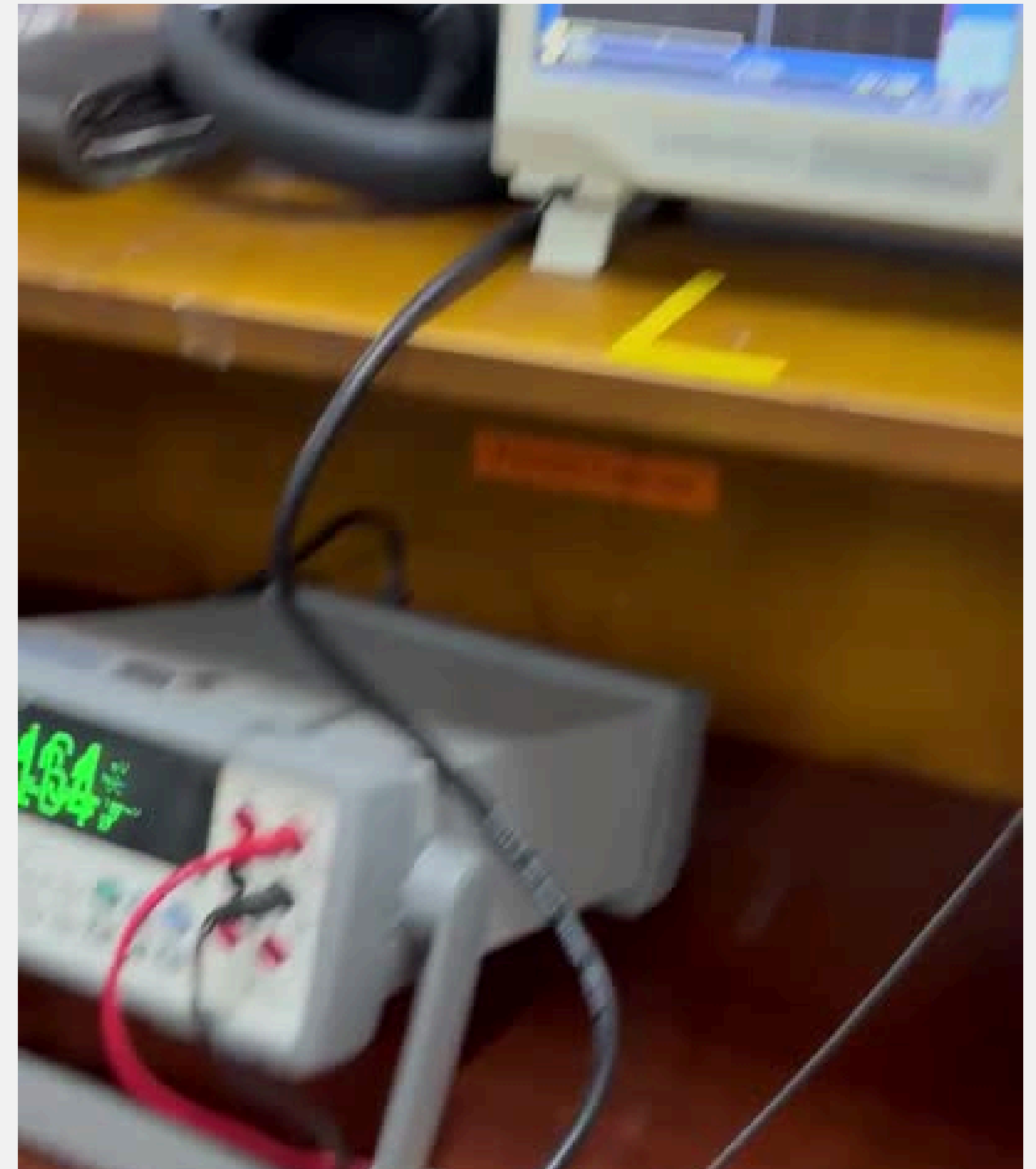



CIRCUIT TESTING

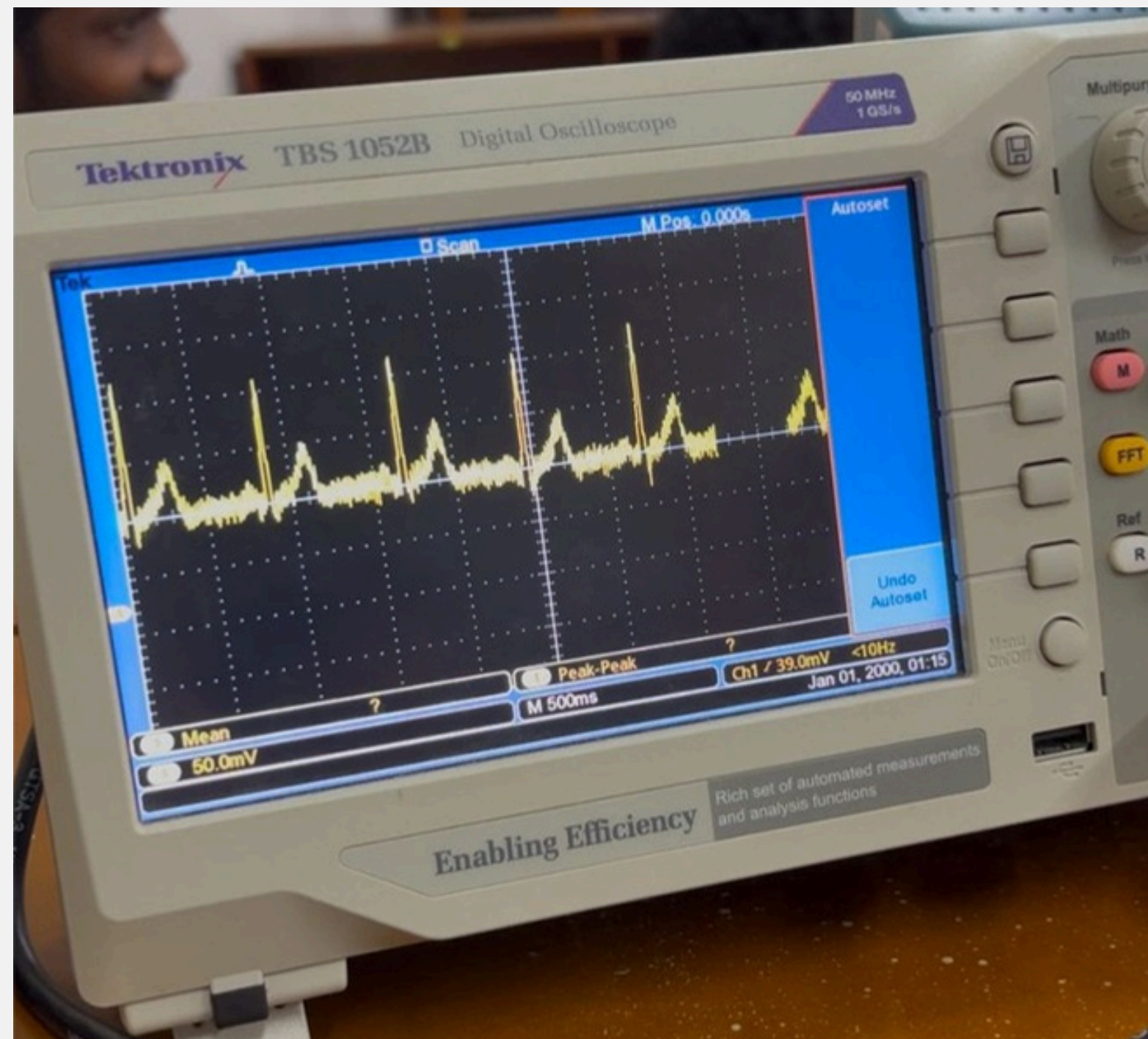



PCB circuit - human testing

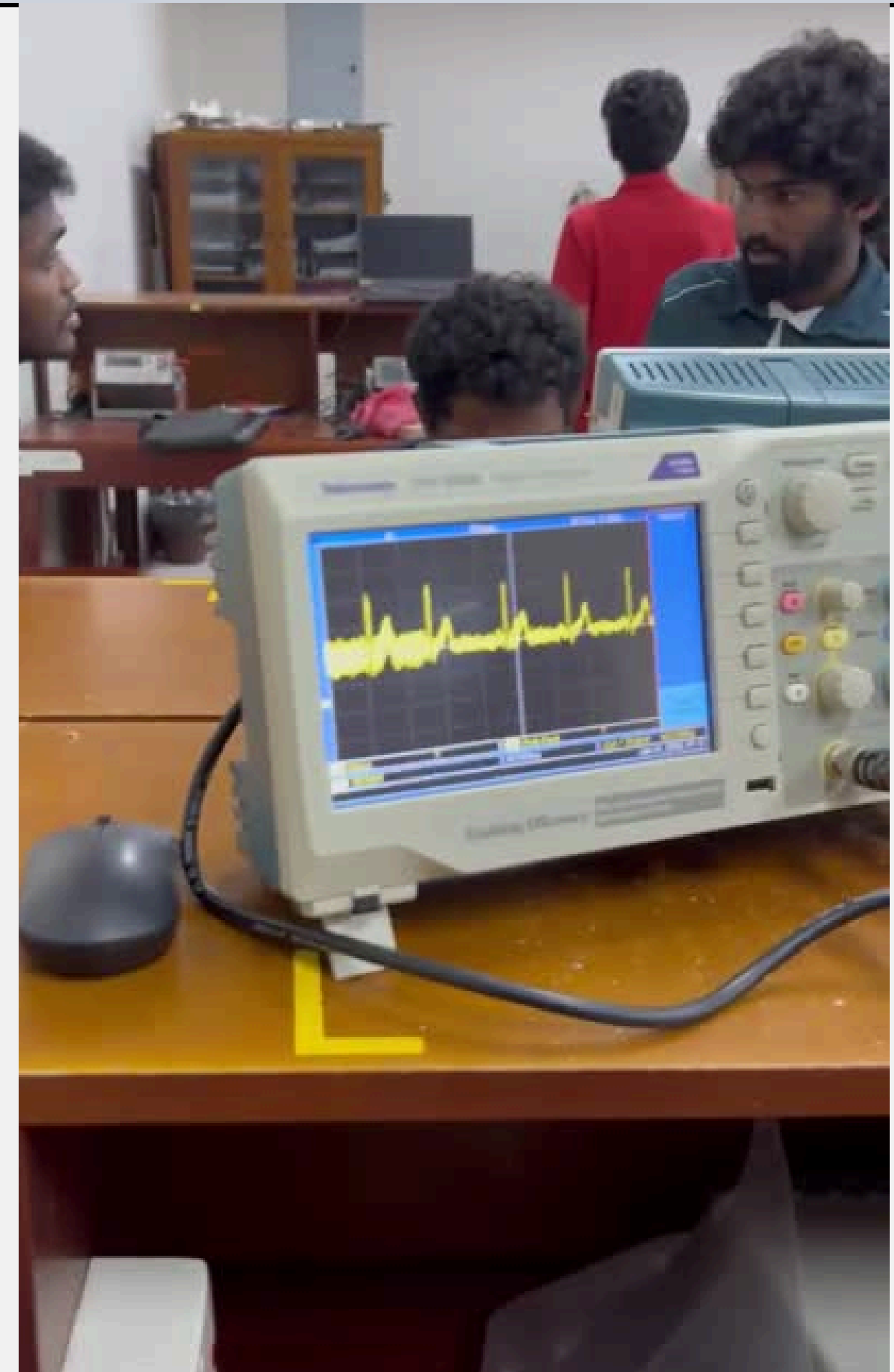

ENCLOSURE

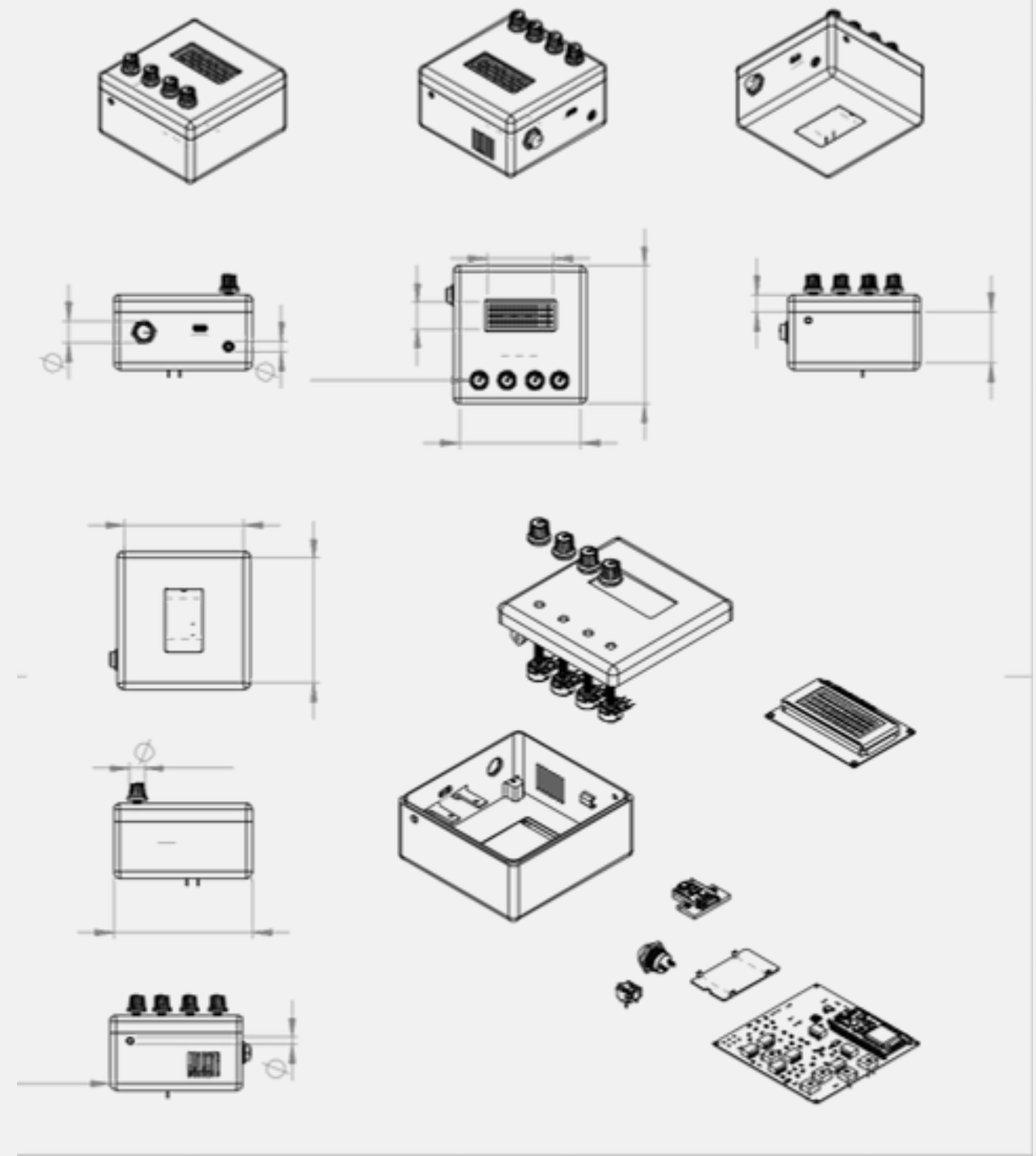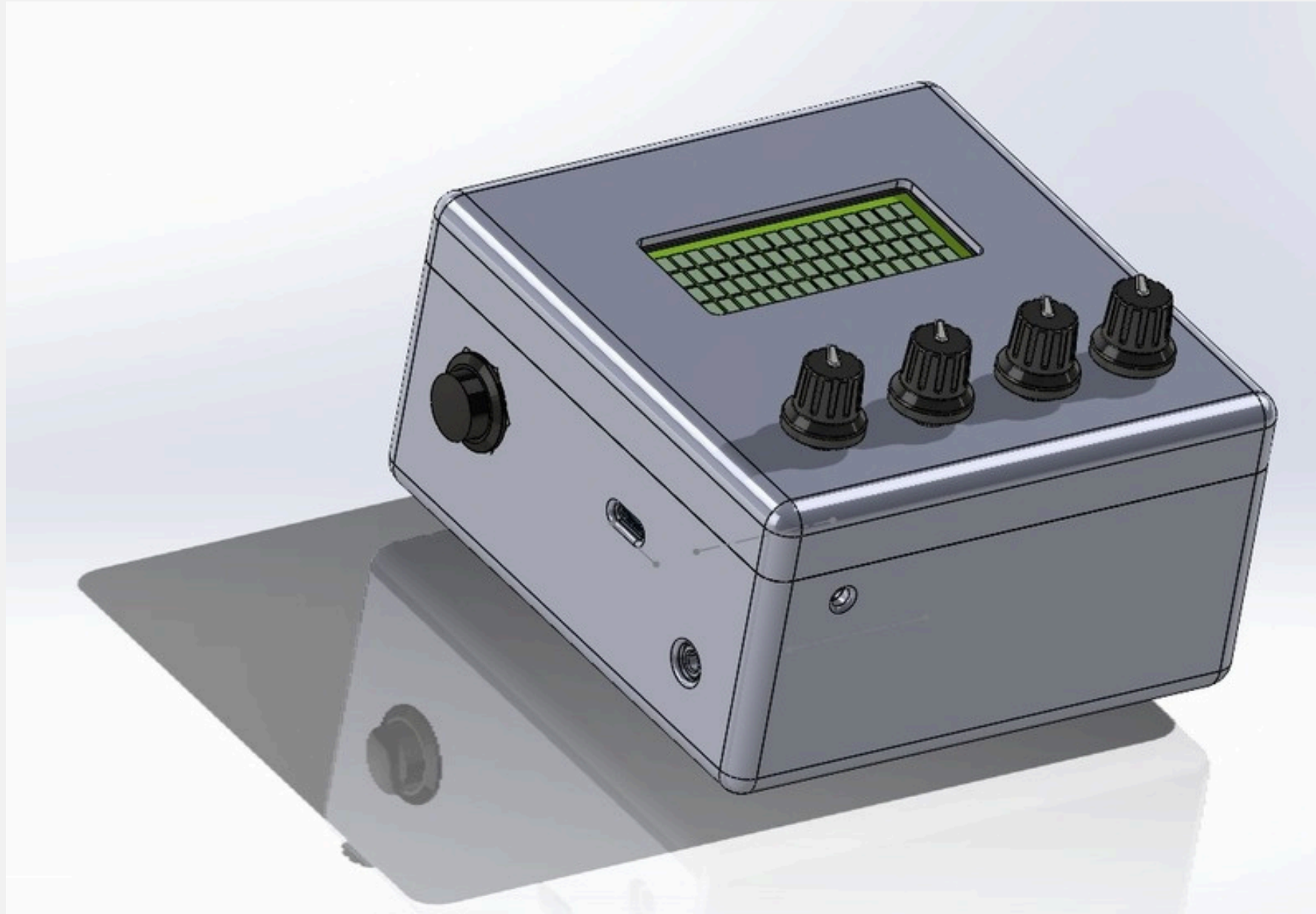

PCB

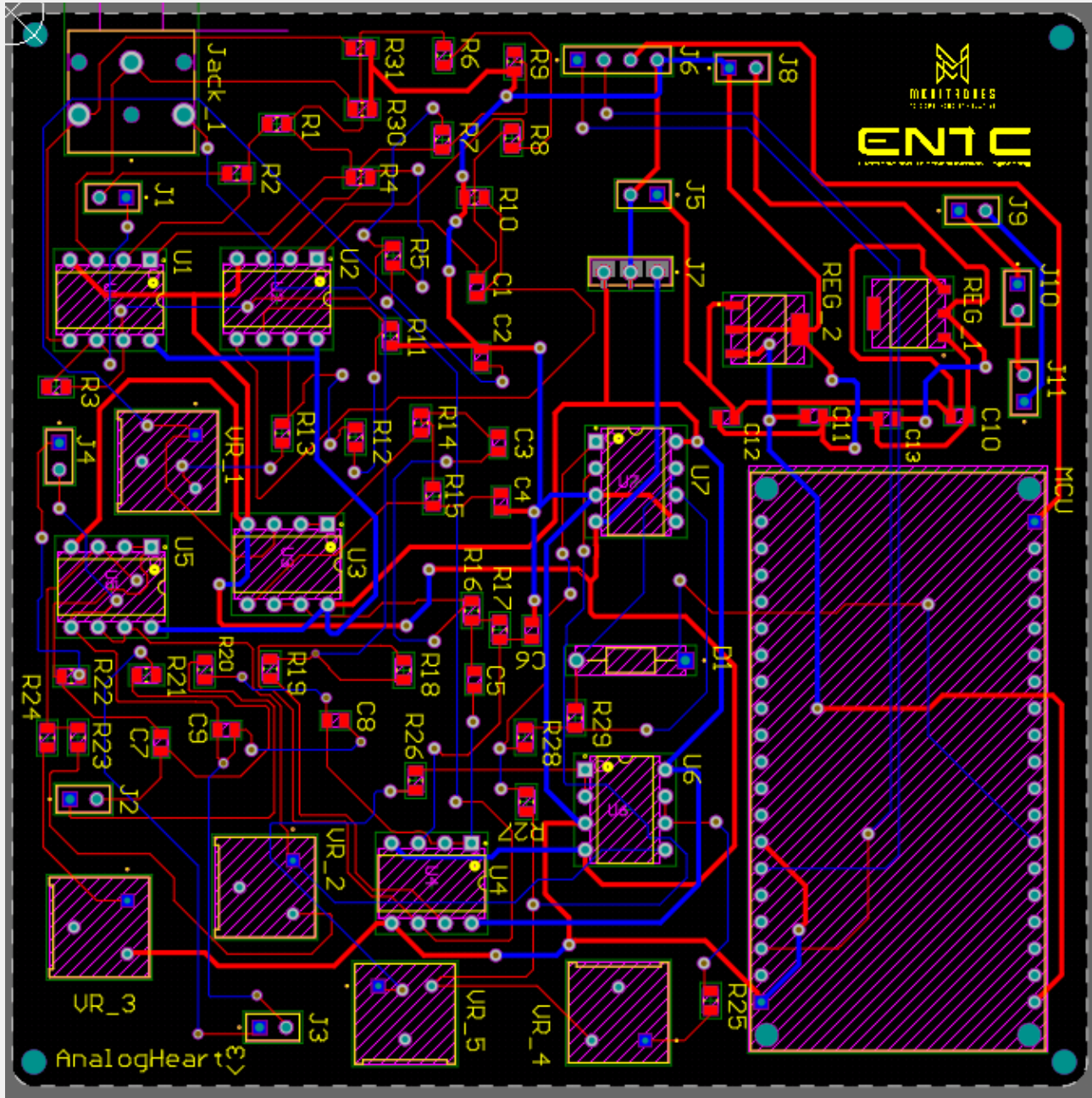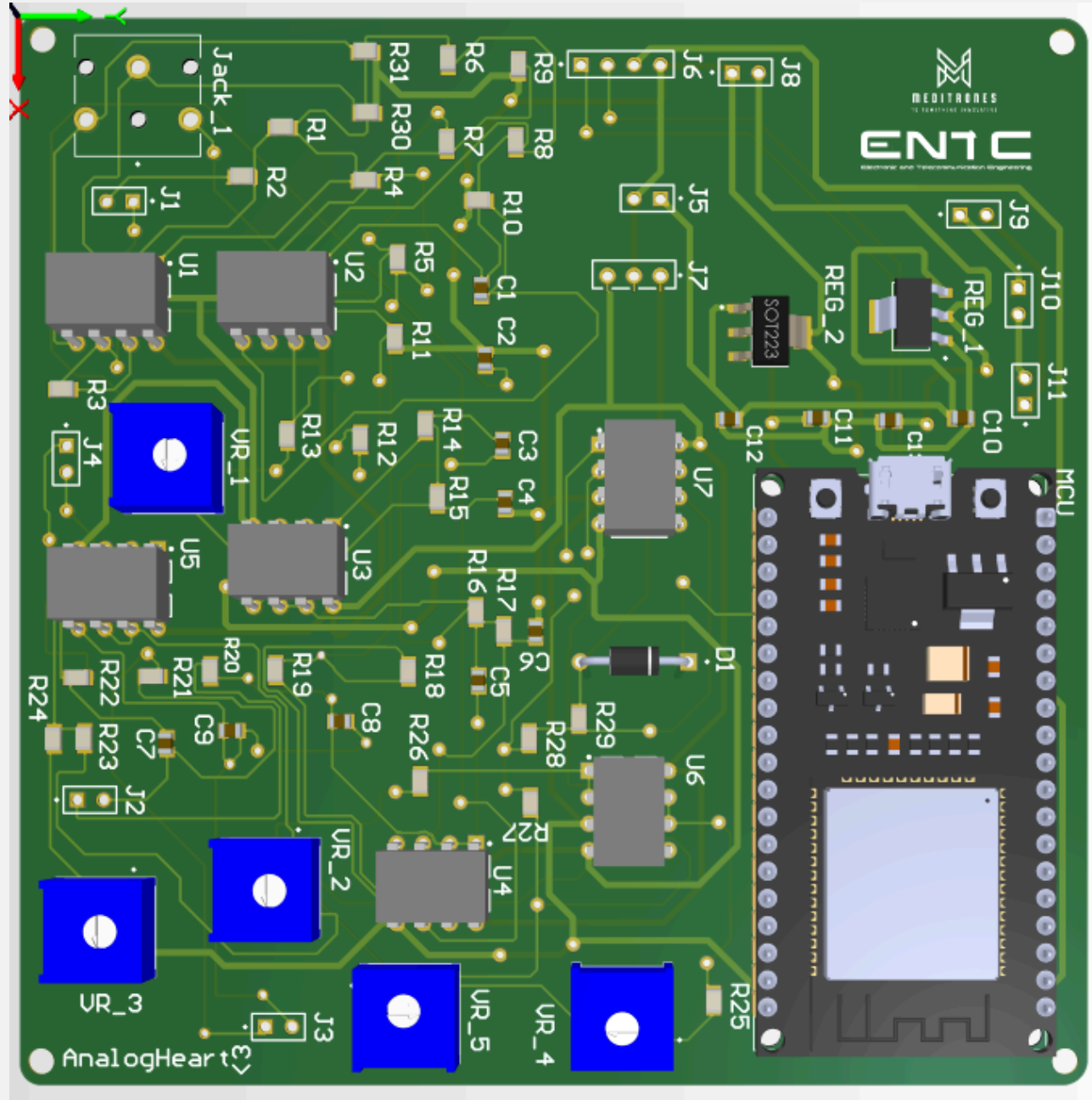

TASK ALLOCATION

- 220005R Aazir M.A.M. - Circuit design and enclosure design
- 220074B Boralugoda M.S. - PCB design and documentation
- 220362G Liyanage D.L.B.B. - Circuit testing and PCB design
- 220374U Madusanka S.P.S. - Enclosure design and Lab Testing

The image features a light blue background with a white rectangular frame. The frame is decorated with stylized, colorful galaxy images. At the top, a large, flowing galaxy structure with blue and yellow hues extends across the width of the frame. At the bottom, several smaller, teardrop-shaped galaxy images, also in blue and yellow, are arranged along the edge. The text "THANK YOU!" is centered within the white frame in a large, bold, black font.

THANK YOU!